

WASHINGTON STATE UNIVERSITY

Power-flow Controls

Power-Flow Controls

1

WASHINGTON STATE UNIVERSITY

Power-Flow Control Devices

- Transformers
 - Tap changing
 - Phase shifting
- Shunt Capacitor/Reactor Banks
- Synchronous Condensers
- Power electronic controls



© Washington State University

2

WASHINGTON STATE UNIVERSITY

Control Devices

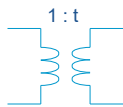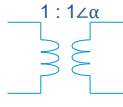- Transformers
 - Tap changing
 - t changes voltage
 - V_{ref} voltage reference
 - Phase shifter
 - α introduces a phase shift
 - MW power-flow depends on angle difference
 - regulates active power-flow





© Washington State University

3


WASHINGTON STATE UNIVERSITY

Control Transformers

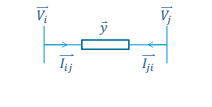

$$\begin{bmatrix} I_{ij} \\ I_{ji} \end{bmatrix} = \begin{bmatrix} \bar{y} & -\bar{y} \\ -\bar{y} & \bar{y} \end{bmatrix} \begin{bmatrix} \bar{V}_i \\ \bar{V}_j \end{bmatrix}$$

$$\bar{V}_s = t\bar{V}_i$$
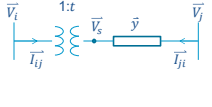
$$\bar{I}_{ji} = (\bar{V}_j - t\bar{V}_i)\bar{y} = -t\bar{y}\bar{V}_i + \bar{y}\bar{V}_j$$


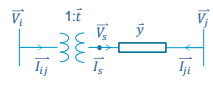
$$\begin{bmatrix} I_{ij} \\ I_{ji} \end{bmatrix} = \begin{bmatrix} |t|^2\bar{y} & -t^*\bar{y} \\ -t\bar{y} & \bar{y} \end{bmatrix} \begin{bmatrix} \bar{V}_i \\ \bar{V}_j \end{bmatrix}$$

© Washington State University

4

WASHINGTON STATE UNIVERSITY

Transformers



$$\begin{aligned} \bar{V}_s \bar{I}_s^* &= \bar{V}_i \bar{I}_{ij}^* \\ \Rightarrow t \bar{V}_i \bar{I}_s^* &= \bar{V}_i \bar{I}_{ij}^* \\ \Rightarrow \bar{I}_{ij} &= t^* \bar{I}_s = -t^* \bar{I}_{ji} \\ \bar{I}_{ji} &= -t\bar{y}\bar{V}_i + \bar{y}\bar{V}_j \\ \bar{I}_{ij} &= |t|^2\bar{y}\bar{V}_i - t^*\bar{y}\bar{V}_j \end{aligned}$$


$$\begin{bmatrix} \bar{I}_{ij} \\ \bar{I}_{ji} \end{bmatrix} = \begin{bmatrix} |t|^2\bar{y} & -t^*\bar{y} \\ -t\bar{y} & \bar{y} \end{bmatrix} \begin{bmatrix} \bar{V}_i \\ \bar{V}_j \end{bmatrix}$$

© Washington State University

5

WASHINGTON STATE UNIVERSITY

Example 1

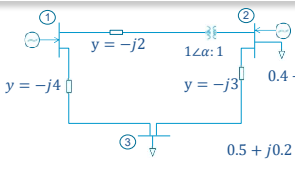

$$i = 2, j = 1$$

$$\bar{t} = 1\angle\alpha, \bar{y} = -j2$$

$$\begin{bmatrix} |t|^2\bar{y} & -t^*\bar{y} \\ -t\bar{y} & \bar{y} \end{bmatrix}$$

$$\bar{Y}_{Bus} = \begin{bmatrix} -j2 - j4 & j2\angle\alpha & j4 \\ j2\angle -\alpha & -j2 - j3 & j3 \\ j4 & j3 & -j4 - j3 \end{bmatrix}$$

$$= \begin{bmatrix} 6\angle -90^\circ & 2\angle(90^\circ + \alpha) & 4\angle 90^\circ \\ 2\angle(90^\circ - \alpha) & 5\angle -90^\circ & 3\angle 90^\circ \\ 4\angle 90^\circ & 3\angle 90^\circ & 7\angle -90^\circ \end{bmatrix}$$

© Washington State University

6

Example 2

$$\vec{Y}_{Bus} = \begin{bmatrix} -j2-j4 & j2 & j4 \\ j2 & -j2-j3 & j3t \\ j4 & j3t & -j4-j3t^2 \end{bmatrix}$$

$$= \begin{bmatrix} 6\angle -90^\circ & 2\angle 90^\circ & 4\angle 90^\circ \\ 2\angle 90^\circ & 5\angle -90^\circ & 3t\angle 90^\circ \\ 4\angle 90^\circ & 3t\angle 90^\circ & (4+3t^2)\angle -90^\circ \end{bmatrix}$$

7

Example 3

$$\vec{Y}_{Bus} = \begin{bmatrix} -j2-j4 & j2\angle\alpha & j4 \\ j2\angle-\alpha & -j2-j3 & j3t \\ j4 & j3t & -j4-j3t^2 \end{bmatrix}$$

$$= \begin{bmatrix} 6\angle -90^\circ & 2\angle(90^\circ + \alpha) & 4\angle 90^\circ \\ 2\angle(90^\circ - \alpha) & 5\angle -90^\circ & 3t\angle 90^\circ \\ 4\angle 90^\circ & 3t\angle 90^\circ & (4+3t^2)\angle -90^\circ \end{bmatrix}$$

8

Control Devices

Capacitor Banks

- Include in the diagonal term \vec{Y}_{ii} in \vec{Y}_{Bus}
- $\Rightarrow Y_{Ci}$ automatically varied to keep $V_i = V_{specified}$
- $\Rightarrow Y_{Ci}$ becomes an unknown $V_i = V_{specified}$

9

Shunt Capacitor banks

- $V_i < V_{refi} \Rightarrow$ switch on capacitors
- $V_i > V_{refi} \Rightarrow$ switch off capacitors
- We may assume $V_i = V_{refi}$ (like a PV bus)

10

Synchronous condensers

- Synchronous machines
- $P_{Gi}=0$ (or small negative) ("motor")
- $V_i < V_{ref} \Rightarrow Q_{gi}$ increased
- $V_i > V_{ref} \Rightarrow Q_{gi}$ decreased
- Q_{gi} adjusted to keep $V_i = V_{refi}$ (PV bus)
- Old generators not efficient to produce active power (Keep exciter circuits)
- Can be used as voltage control device; Synchronous condenser

11

Power electronic controls

- Static VAR Compensator (SVC)
- Static Synchronous Compensator (STATCOM)
- Thyristor Controlled Series Compensation (TCSC)

12