

WASHINGTON STATE UNIVERSITY

## EE 491: Review of EE361

### Transmission Line Models Review

1

WASHINGTON STATE UNIVERSITY

## Homework 1

- Due on Sept 3 2020 @ 9 am

Per Unit Problem:

Common MVA Base should be specified.  
You can use either **30 MVA Base** or **100 MVA Base**.

© Washington State University

2

WASHINGTON STATE UNIVERSITY

## Basics

$$v(t) = \sqrt{2}V \cos(\omega t) \quad \vec{V} = V \angle 0$$

$$i(t) = \sqrt{2}I \cos(\omega t - \varphi) \quad \vec{I} = I \angle -\varphi$$

$$p(t) = 2VI \cos(\omega t) \cos(\omega t - \varphi)$$

$$= 2VI \cos(\omega t) (\cos \omega t \cos \varphi + \sin \omega t \sin \varphi)$$

$$= VI \cos \varphi [2 \cos^2 \omega t] + VI \sin \varphi [2 \cos \omega t \sin \omega t]$$

$$= VI \cos \varphi [1 + \cos 2\omega t] + VI \sin \varphi [\sin 2\omega t]$$

$$= P [1 + \cos 2\omega t] + Q [\sin 2\omega t]$$

$$= p_1(t) + p_2(t)$$

© Washington State University

3

WASHINGTON STATE UNIVERSITY

## Basics

Assume  $V=1$ ,  $\varphi=60^\circ$ . Then,  $P=0.5$ ,  $Q=0.877$

Average = 0.5.  
Real power.

Average = 0.  
Swinging power.

© Washington State University

4

WASHINGTON STATE UNIVERSITY

## Basics

$$\vec{V} = V \angle 0 \quad \vec{I} = I \angle -\varphi$$

$$\vec{S} = \vec{V} \vec{I}^* = VI \cos \varphi + j VI \sin \varphi = P + j Q$$

- $P = VI \cos \varphi$  and  $Q = VI \sin \varphi$
- $S = P + j Q$
- Real power well-understood.
- Generators are sources. Loads and Losses are sinks.
- Reactive power?

© Washington State University

5

WASHINGTON STATE UNIVERSITY

## Basic components

$$\vec{I} = \frac{V \angle 0}{R} = \frac{V}{R} \angle 0$$

$$S = \vec{V} \vec{I}^* = V \angle 0 \left( \frac{V}{R} \angle 0 \right)^* = \frac{V^2}{R} + j 0$$


$$P = \frac{V^2}{R} \quad Q = 0$$

Resistors are sinks of real power

© Washington State University

6


### Reactive power

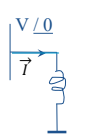

$$\vec{I} = \frac{V\angle 0}{jx} = \frac{V}{x}\angle -90^\circ$$

$$S = \vec{V} \vec{I}^* = V\angle 0 \left( \frac{V}{x}\angle -90^\circ \right)^* = 0 + j\frac{V^2}{x}$$

$$P = 0 \quad Q = \frac{V^2}{x}$$




Reactors  
are sinks of  
reactive  
power

© Washington State University

7


### Reactive power

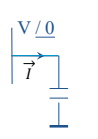

$$\vec{I} = jy * V\angle 0 = Vy\angle 90^\circ$$

$$S = \vec{V} \vec{I}^* = V\angle 0 (Vy\angle 90^\circ)^* = 0 - jV^2y$$

$$P = 0 \quad Q = -V^2y$$




Capacitors  
are sources  
of reactive  
power

© Washington State University

8
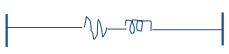
### Real power management

- Generators are sources.
- Loads and MW losses are sinks.
- MW losses small.
- Can transfer MW power over long distances.
- Thermal limits.




© Washington State University

9

### Reactive power management


- Generators and capacitors are sources.
- Reactors and loads are sinks.
- Abundance of reactors in the power system.
- Line reactances typically ten times the line resistances. Same for transformers,...




© Washington State University

10

### Transmission Line Model



unit length

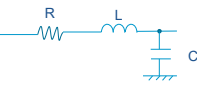

$$L \approx C_1 \ln C_2 \frac{D}{r}$$

$$C \approx \frac{1}{C_3 \ln C_4 \frac{D}{r}}$$

$$R \approx \frac{1}{Area}$$

$$\omega L \approx 0.5 \text{ } \Omega/\text{mile}$$

$$\omega C \approx 10^{-5} \text{ S/mile}$$


$$R \approx 0.05 \text{ } \Omega/\text{mile}$$

© Washington State University

11

### Transmission Line Models

Distributed Parameter Circuit



Line Model

Short  
 $\ell < 50 \text{ miles}$

Medium  
 $50 \text{ miles} < \ell < 150 \text{ miles}$


Long  
 $\ell > 150 \text{ miles}$

© Washington State University

12

### Transmission Line Model

WASHINGTON STATE UNIVERSITY

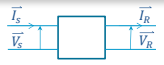

$$\begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \bar{V}_R \\ \bar{I}_R \end{bmatrix}$$

$$\begin{aligned} \bar{I}_a &= I \angle (-\varphi) \\ \bar{I}_b &= I \angle (-\varphi - 120^\circ) \\ \bar{I}_c &= I \angle (-\varphi + 120^\circ) \end{aligned}$$

$$\bar{S}_a = \bar{V}_a \bar{I}_a^* = VI \angle (\varphi) = P_a + jQ_a$$

$$\bar{S} = \bar{S}_a + \bar{S}_b + \bar{S}_c = 3VI \angle (\varphi) = P + jQ \quad (\text{normally used for Rating})$$

$$P = 3VI \cos \varphi = \sqrt{3} V_L I_L \cos \varphi$$


$$Q = 3VI \sin \varphi = \sqrt{3} V_L I_L \sin \varphi$$

© Washington State University 13

13

### Short Line Model


WASHINGTON STATE UNIVERSITY

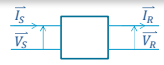

$$\begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \bar{V}_R \\ \bar{I}_R \end{bmatrix}$$

Short line:  $l < 50$  miles

Ignore all capacitances

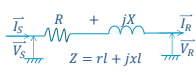

$$\bar{V}_S = \bar{V}_R + Z \bar{I}_R$$

$$\begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \bar{V}_R \\ \bar{I}_R \end{bmatrix}$$

$$\bar{V}_S = \bar{V}_R + R \bar{I}_R + jX \bar{I}_R$$

© Washington State University 14


14

### Medium Line Model

WASHINGTON STATE UNIVERSITY

Medium line:  $50 \text{ miles} < l < 150 \text{ miles}$

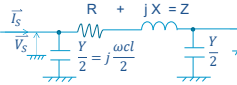Lump all capacitances  $\Rightarrow$  Put one half on each side



$$\begin{aligned} R &= rl \\ X &= xl = \omega Ll \\ Y &= yl = \omega Cl \end{aligned}$$

$$\bar{I}_1 = \bar{I}_R + \bar{V}_R \frac{Y}{2}$$

$$\begin{aligned} \bar{V}_S &= \bar{V}_R + Z \bar{I}_1 \\ &= \bar{V}_R + Z \bar{I}_R + \frac{ZY}{2} \bar{V}_R \\ &= \left(1 + \frac{ZY}{2}\right) \bar{V}_R + Z \bar{I}_R \end{aligned}$$

© Washington State University 15

15

### Medium Line Model

WASHINGTON STATE UNIVERSITY

$$\begin{aligned} \bar{I}_S &= \bar{I}_1 + \bar{V}_S \frac{Y}{2} = \bar{I}_R + \bar{V}_R \frac{Y}{2} + \frac{Y}{2} \left(1 + \frac{ZY}{2}\right) \bar{V}_R + \frac{Y}{2} Z \bar{I}_R \\ &= \bar{V}_R \left(\frac{Y}{2} + \frac{Y}{2} + \frac{Y^2 Z}{4}\right) + \bar{I}_R \left(1 + \frac{YZ}{2}\right) \\ &= \bar{V}_R \left(Y + \frac{Y^2 Z}{4}\right) + \bar{I}_R \left(1 + \frac{YZ}{2}\right) \end{aligned}$$

$$\begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix} = \begin{bmatrix} 1 + \frac{YZ}{2} & Z \\ Y \left(1 + \frac{YZ}{4}\right) & 1 + \frac{YZ}{2} \end{bmatrix} \begin{bmatrix} \bar{V}_R \\ \bar{I}_R \end{bmatrix}$$


© Washington State University 16

16
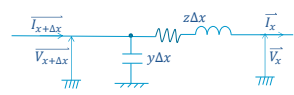
### Long Line Model

WASHINGTON STATE UNIVERSITY

Long line:  $l > 150$  miles  $\Rightarrow$  Distributed Parameter Circuit



$$\begin{aligned} \bar{I}_{x+\Delta x} &= \bar{I}_x + y \Delta x \bar{V}_x \Rightarrow \frac{\Delta \bar{I}_x}{\Delta x} = y \bar{V}_x \\ \bar{V}_{x+\Delta x} &= \bar{V}_x + z \Delta x \bar{I}_x \Rightarrow \frac{\Delta \bar{V}_x}{\Delta x} = z \bar{I}_x \end{aligned}$$

© Washington State University 17


17

### Long Line Model

WASHINGTON STATE UNIVERSITY

$$\begin{aligned} \frac{d\bar{I}_x}{dx} &= y \bar{V}_x \Rightarrow \frac{d^2 \bar{V}_x}{dx^2} = yz \bar{V}_x \\ \frac{d\bar{V}_x}{dx} &= z \bar{I}_x \Rightarrow \frac{d^2 \bar{I}_x}{dx^2} = yz \bar{I}_x \end{aligned}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh \gamma l & Z_c \sinh \gamma l \\ \frac{1}{Z_c} \sinh \gamma l & \cosh \gamma l \end{bmatrix}$$
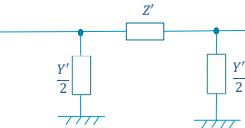
$$Z_c = \sqrt{\frac{z}{y}} \quad \& \quad \gamma = \sqrt{zy}$$


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + \frac{z' y' l^2}{2} & Z' \\ y' \left(1 + \frac{z' y' l^2}{4}\right) & 1 + \frac{z' y' l^2}{2} \end{bmatrix}$$

© Washington State University 18

18



WASHINGTON STATE  
UNIVERSITY

## Book Problem 6.5

**Capacitive Reactance:**  $x_c = x_a' + x_d'$

From Table A.3:  $x_a' = 0.1057 \text{ M}\Omega/\text{mile}$

From Table A.5:  $x_d' = 0.0858 + \frac{0.0016}{10} \times 9 = 0.0872 \text{ M}\Omega/\text{mile}$

$\Rightarrow x_c = 0.1929 \text{ M}\Omega/\text{mile}$

$\Rightarrow y_c = 0.5184 \times 10^{-5} \text{ S}/\text{mile}$

2)  $Z = (0.3372 + j0.8146) \Omega/\text{mile} \times 70 \text{ mile}$


$Y = 70 \frac{1}{0.1929 \times 10^6} \text{ S} = 3.6288 \times 10^{-4} \text{ S}$

© Washington State University 25

25

WASHINGTON STATE  
UNIVERSITY

## Book Problem 6.5

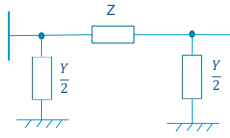

$Z = (0.3372 + j0.8146) \Omega/\text{mile} \times 70 \text{ mile}$

$Y = 70 \frac{1}{0.1929 \times 10^6} \text{ S} = 3.6288 \times 10^{-4} \text{ S}$

© Washington State University 26

26