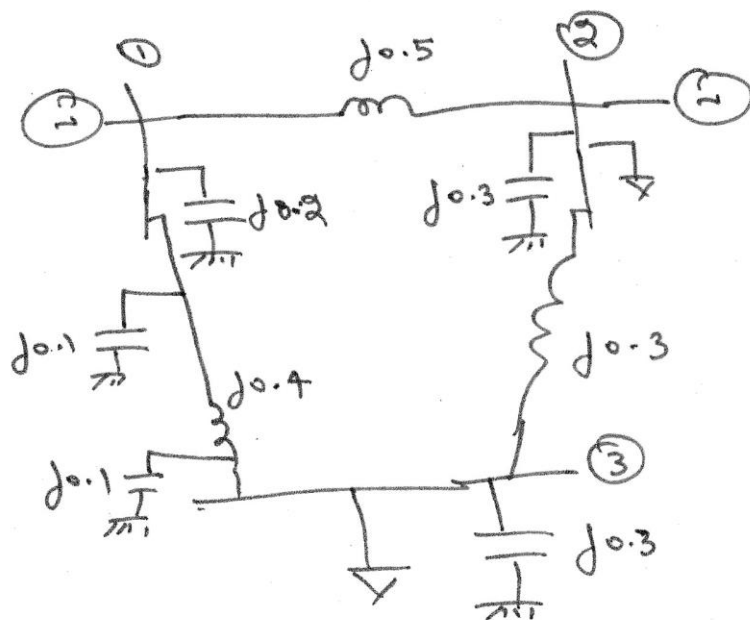


EE491 Homework 3


Due September 17 2020 at 9 am

Find Y_{BUS} matrices for the following four power systems after first recognizing impedances from admittances in the values shown.


1)



2)

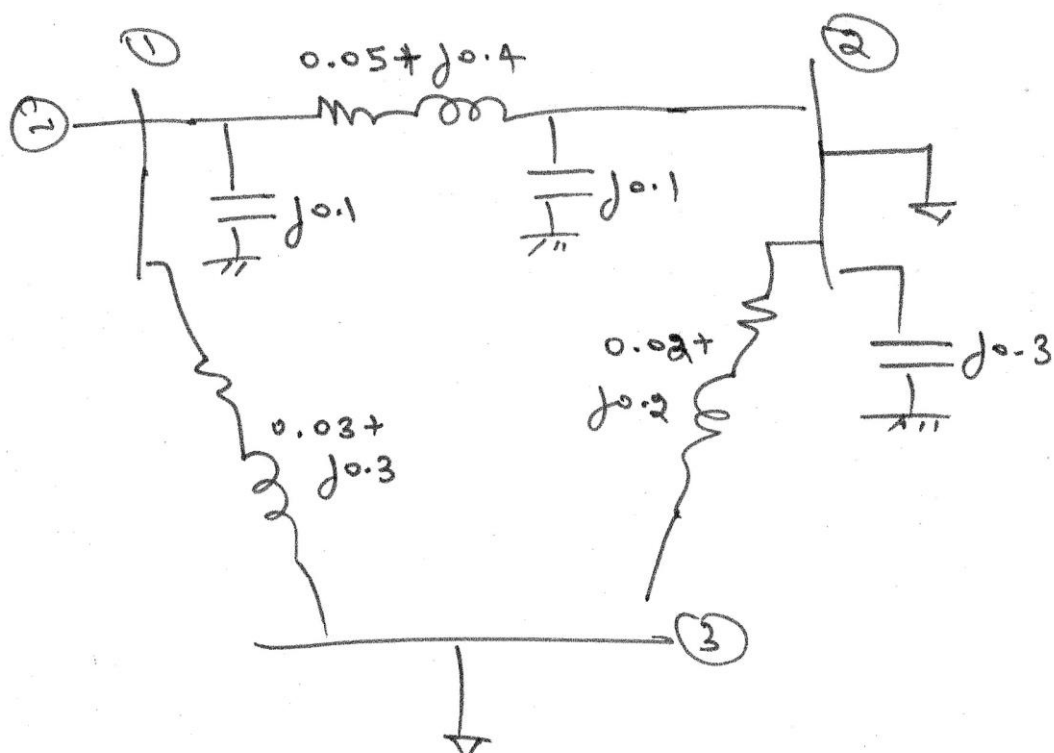

3

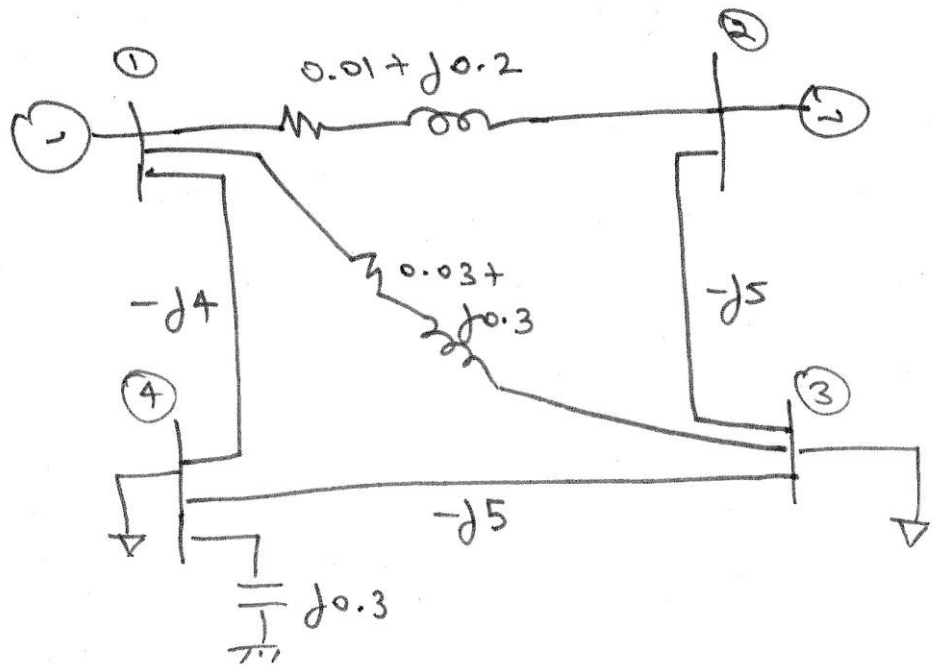

4

