

WASHINGTON STATE UNIVERSITY

## Power-Flow Analysis


Admittance Matrix Representation

1

WASHINGTON STATE UNIVERSITY

## Radial Network Analysis

Individual transmission line models

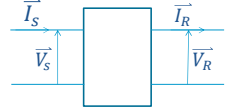

$$\begin{bmatrix} \vec{V}_S \\ \vec{I}_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \vec{V}_R \\ \vec{I}_R \end{bmatrix}$$

© Washington State University


2

WASHINGTON STATE UNIVERSITY

## Meshed Network Analysis

Admittance representation easier.  
Ybus formulation.  
Main difference: Current injection at all buses.

$$\vec{I}_{bus} = \begin{bmatrix} \vec{I}_1 \\ \vdots \\ \vec{I}_N \end{bmatrix} \quad \text{injection} \quad \vec{V}_{bus} = \begin{bmatrix} \vec{V}_1 \\ \vdots \\ \vec{V}_N \end{bmatrix}$$

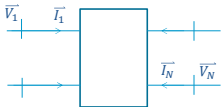
$$\vec{I}_{bus} = \vec{Y}_{bus} \vec{V}_{bus}$$


© Washington State University

3

WASHINGTON STATE UNIVERSITY

## Admittance Analysis

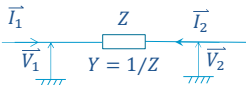

$$\vec{I}_1 = \frac{\vec{V}_1 - \vec{V}_2}{Z} = \frac{\vec{V}_1}{Z} - \frac{\vec{V}_2}{Z}$$

$$\vec{I}_2 = \frac{\vec{V}_2 - \vec{V}_1}{Z} = \frac{\vec{V}_2}{Z} - \frac{\vec{V}_1}{Z}$$


$$\begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} Y & -Y \\ -Y & Y \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}$$

© Washington State University

4

WASHINGTON STATE UNIVERSITY

## Network Analysis

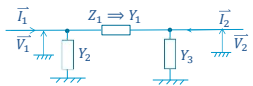

$$\vec{I}_1 = (\vec{V}_1 - \vec{V}_2)Y_1 + \vec{V}_1Y_2$$

$$\vec{I}_2 = (\vec{V}_2 - \vec{V}_1)Y_1 + \vec{V}_2Y_3$$

$$\vec{I}_1 = \vec{V}_1(Y_1 + Y_2) + \vec{V}_2(-Y_1)$$

$$\vec{I}_2 = \vec{V}_1(-Y_1) + \vec{V}_2(Y_1 + Y_3)$$

$$\begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} Y_1 + Y_2 & -Y_1 \\ -Y_1 & Y_1 + Y_3 \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}$$

© Washington State University

5

WASHINGTON STATE UNIVERSITY

## Network Analysis

$$\vec{I}_{bus} = \vec{Y}_{bus} \vec{V}_{bus}$$

$\vec{Y}_{ij}$  = Off-diagonal entry  
= -Net admittance between Buses i and j


$\vec{Y}_{ii}$  = Diagonal entry  
= Sum of all admittances connected to Bus i

$$\vec{Y}_{bus} = \begin{bmatrix} Y_1 + Y_2 & -Y_1 \\ -Y_1 & Y_1 + Y_3 \end{bmatrix}$$

© Washington State University

6

## Example 1

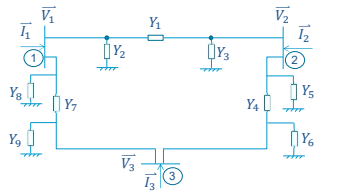


Step 1: Convert all impedances to Admittances.  
Step 2: use the rule to write out the  $\bar{Y}_{bus}$  matrix.

© Washington State University

7

7

## Example 1

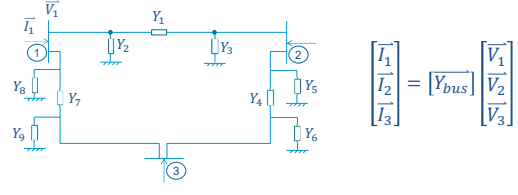

$$\begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \\ \bar{I}_3 \end{bmatrix} = [\bar{Y}_{bus}] \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \\ \bar{V}_3 \end{bmatrix}$$


$$\bar{Y}_{bus} = \begin{bmatrix} Y_1 + Y_7 + Y_2 + Y_8 & -Y_1 & -Y_7 \\ -Y_1 & Y_1 + Y_4 + Y_3 + Y_5 & -Y_4 \\ -Y_7 & -Y_4 & Y_4 + Y_7 + Y_6 + Y_9 \end{bmatrix}$$

© Washington State University

8

8

## Example 2

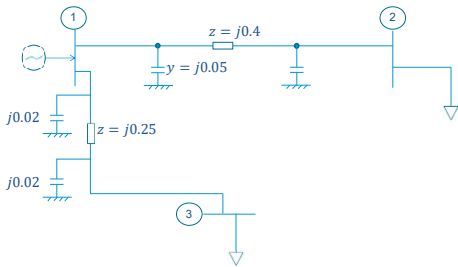


© Washington State University

9

9

## Example 2

Step 1:

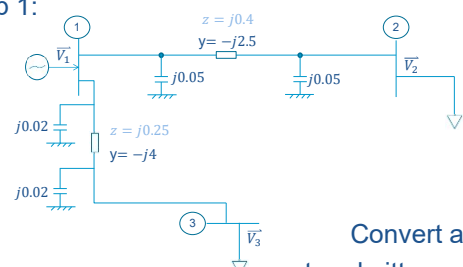


Convert all  
to admittances

© Washington State University

10

10

## Example 2

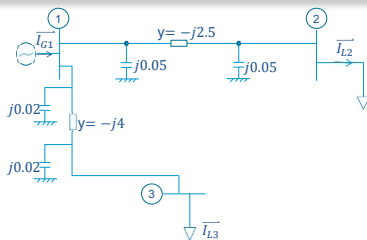

$$\begin{aligned} \bar{I}_1 &= \bar{I}_{G1} \\ \bar{I}_2 &= -\bar{I}_{L2} \\ \bar{I}_3 &= -\bar{I}_{L3} \end{aligned}$$

$$\bar{Y}_{bus} = \begin{bmatrix} -j2.5 - j4 + j0.05 + j0.02 & j2.5 & j4 \\ j2.5 & -j2.5 + j0.05 & 0 \\ j4 & 0 & -j4 + j0.02 \end{bmatrix}$$

© Washington State University

11

11