

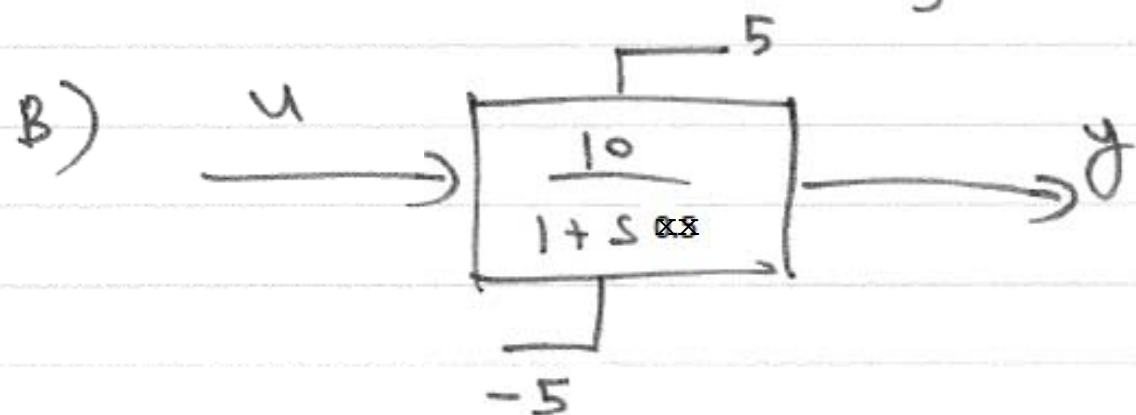
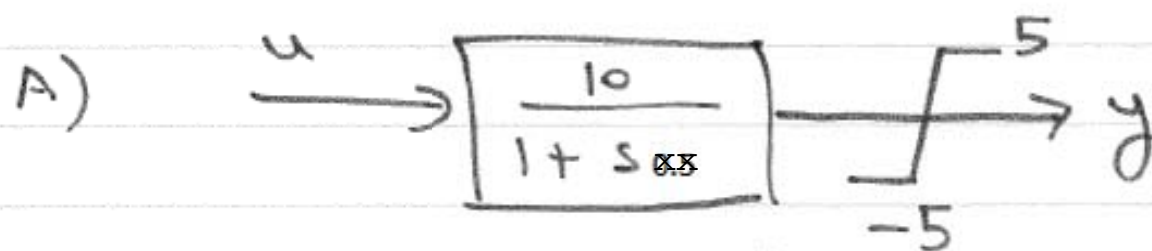


Consider The two amplifiers below.

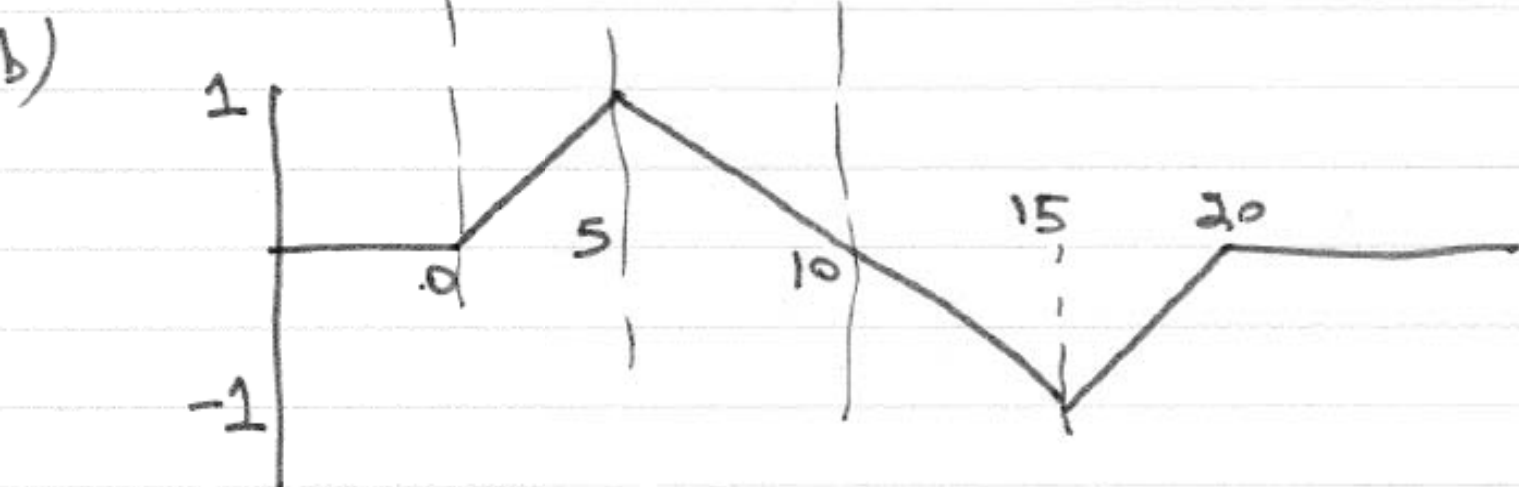

Consider two different inputs:

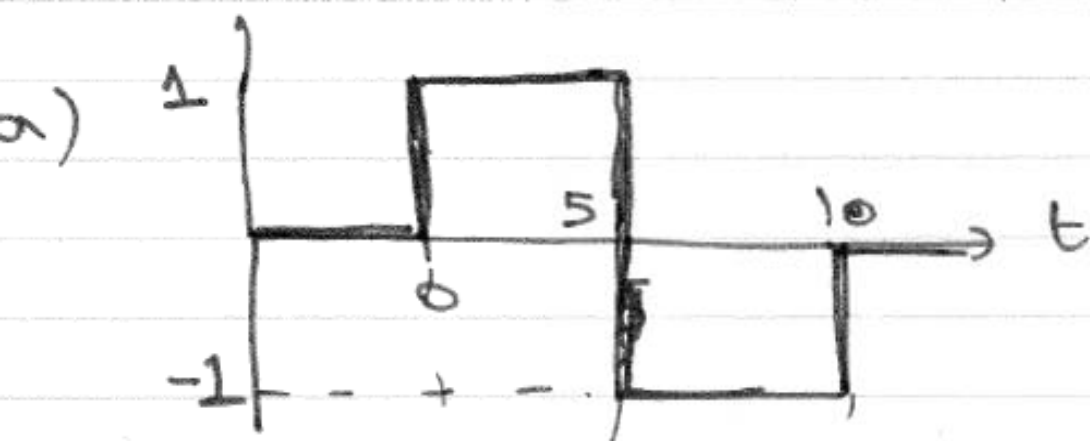

Simulate the outputs of amplifiers A and B for the inputs a and b. Discuss your results.