

$$\omega_n = \frac{1}{\sqrt{LC}} = 2533.5 \text{ rad/s} \quad (1)$$

$$\zeta = \frac{r_L}{2 * \sqrt{\frac{L}{C}}} = 0.0104 \quad (2)$$

$$\omega_d = \omega_n \sqrt{1 - \zeta^2} = 2533.3 \text{ rad/s} \quad (3)$$

$$Q_{factor, seriesRLC} = \frac{\omega_n L}{R} = 48.136 \quad (4)$$

$$Q_{3ph} = 3 * V_{ph} * (|I_{ph}|)^2 * X_{ph} = -602.04 \text{ kVAr} \quad (5)$$

$$\lambda = \{-26.316 \pm 2533\} \tau = \frac{L}{r_L} = 0.038 \text{ s} \quad (6)$$

$$\text{KVL:} \quad V_{dc} = r_L i_L + L \dot{i}_L + v_C \quad (7)$$

$$\Rightarrow \quad \boxed{\dot{i}_L = \frac{1}{L} (-r_L i_L - v_C + V_{dc})} \quad (1)$$

$$\text{Capacitor:} \quad i_L = C \dot{v}_C \Rightarrow \quad \boxed{\dot{v}_C = \frac{1}{C} i_L} \quad (2)$$

$$\ddot{i}_L = \frac{1}{L} (-r_L \dot{i}_L - \dot{v}_C) = -\frac{r_L}{L} \dot{i}_L - \frac{1}{LC} i_L$$

$$\boxed{\ddot{i}_L + \frac{r_L}{L} \dot{i}_L + \frac{1}{LC} i_L = 0}$$

Characteristic polynomial and comparison with the canonical 2nd-order form:

$$s^2 + \frac{r_L}{L} s + \frac{1}{LC} = 0 \quad \Longleftrightarrow \quad s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$\boxed{\omega_n = \frac{1}{\sqrt{LC}}, \quad \zeta = \frac{r_L}{2} \sqrt{\frac{C}{L}}}$$