

Lab Assignment 8: MOSFET Amplifier Circuits

Revision: March 20, 2023

Summary

Practical MOSFET circuits are not only used in discrete electronic circuits, they are also the driving force behind digital and analog VLSI design. In this lab, you will design, simulate and experimentally validate a single stage common source MOSFET amplifier as an example of a discrete amplifier circuit. Then, you will design a current mirror source using ZVN3310 MOSFET transistors; current mirrors are used as biasing circuits within analog VLSI systems. Then, you will build a CMOS inverter using complementary NMOS and PMOS transistors to determine its voltage transfer curve, and finally you will properly bias the inverter to make it work as a single stage CMOS amplifier.

Learning Outcomes: After completing this lab, you should be able to:

- Design, simulate and analyze single stage common source MOSFET amplifiers.
- Design and build a CMOS current mirror source.
- Build and test a CMOS inverter.
- Properly bias the CMOS inverter to work as a single stage CMOS amplifier.

Required Equipment

- EE352 analog parts kit
- Breadboard
- Function generator, oscilloscope
- DMM
- DC power supplies

I. Single Stage Common Source Amplifier

Figure 1 shows a single stage common source MOSFET amplifier circuit. We wish to design the circuit to meet the following design specifications:

Load Resistance: $R_L = 100 \text{ K } \Omega$

Input Resistance: $R_i > 200 \text{ K } \Omega$

Mid-band Gain: $G_v = V_o/V_i = -50 \pm 20\%$

Supply Voltage: +15 Volts

Circuit Capacitors: $C_G = 10 \text{ } \mu\text{F}$; $C_S = 47 \text{ } \mu\text{F}$; $C_D = 10 \text{ } \mu\text{F}$

 


Figure 1. Common Source MOSFET Amplifier

Pre-lab:

- (a) Design the amplifier to meet the specifications above by choosing values for resistors R_1 , R_2 , R_D and R_S . Begin your design by choosing an appropriate value for the bias current I_D . If $I_D \approx 0.3 \text{ mA}$, assume $V_T \approx 1.7 \text{ V}$, $K_n \approx 0.02 \text{ A/V}^2$ and $V_A = 100 \text{ V}$ ($\lambda = 0.01 \text{ V}^{-1}$). Find the small signal approximation of the input resistance R_{in} where

$$R_{in} = R_1 \parallel R_2. \quad (1)$$

Find the small signal approximation of the output resistance R_o , where R_o is given as

$$R_o = R_D \parallel R_L \parallel r_o. \quad (2)$$

The small signal mid-band gain of the amplifier is given by

Lab Assignment 8: MOSFET Amplifier Circuits

$$G_v = -g_m R_o \quad (3)$$

where

$$g_m = \sqrt{2k_n I_D} = k_n (V_{GS} - V_T). \quad (4)$$

Once you choose I_D the DC biasing of the transistor can be found using simple rules of thumb. The voltage V_G should be approximately equal to $V_{DD}/3 > V_T$. For maximum symmetry, V_D should be biased at the midpoint between V_D (Max) and V_D (Min). Clearly, the maximum V_D is V_{DD} and the minimum $V_D > V_G - V_T$. For example, if $V_T = 1.7$ V and $V_G = 1/3 V_{DD} = 5$ V, then $V_D \approx 9$ V for maximum symmetry.

- (b) Using PSPICE (LTSPICE or Orcad), simulate the circuit using $V_T \approx 1.7$ V, $K_n \approx 0.02$ V/A and $V_A = 100$ V ($\lambda = 0.01$ V⁻¹). The simulation should include an AC sweep of the gain in dB and the simulation should show the low cut-off frequency, the midband gain (100 Hz to 10 Meg Hz). In your simulation, you may adjust the values of R_S and R_D until the gain is -50 V/V.

Hint: When using MOSFETs, decreasing the current by increasing R_S allows you to increase R_D , which increases the gain of the amplifier.

Lab Procedures:

1. Measure all resistors with your DMM and record their values in your lab notebook. Use the RLC meter to measure the exact capacitance values.
2. With no AC signal applied to the circuit, apply the DC supply voltage. Then measure and record all DC voltages in the circuit with your DMM. At this point, your DC measurements should be very close to your expected DC values. Then, estimate the value of g_m from your DC measurements, using equation (4) above.
3. Apply a 20 mV peak-to-peak sinusoidal input signal at 20 kHz. Measure the output voltage with your oscilloscope. Compute the midband gain. If the gain is not within the specs of -50 V/V $\pm 20\%$, then adjust R_S and R_D as needed. To increase the gain, increase both R_S and R_D by a factor of α in order to increase the gain by $\sqrt{\alpha}$ and vice versa.
4. *Demonstrate your circuit to the TA and have him or her initial your lab checklist.*
5. Determine the low cutoff frequency (f_L) and the high cutoff frequency (f_H) of the amplifier. To determine f_L , measure V_o at the midband (20 kHz), then decrease the frequency until the output voltage is 0.707 ($1/\sqrt{2}$) of V_o at the midband. This is the low cutoff frequency; record this frequency in your notebook. To determine f_H , increase the frequency until the output voltage is 0.707 ($1/\sqrt{2}$) of V_o at the midband. This is the high cutoff frequency; record this frequency in your notebook.

Lab Assignment 8: MOSFET Amplifier Circuits

6. Plot the frequency response of your amplifier (i.e., plot the gain in dB vs. log10 of the frequency). Start from two decades below f_L up to two decades after f_H . Make sure to have enough pts around f_L and f_H to capture the curve smoothly. It is recommended that you plot the data on Matlab or MS Excel as you collect the data. This shows the smooth curve as you are collecting the data. Include the frequency response plot in your lab report.
7. *Demonstrate your frequency response plot to the TA and have him or her initial your lab checklist.*
8. Increase the amplitude of the input signal until the output voltage is clipping at the top and the bottom. Measure the clipping voltage at the drain of the transistor, using DC coupling. Include the plot of the clipping voltage in your report.

II. Current Mirror Circuit

In analog VLSI design, amplifiers are biased using current mirror sources due to their efficient structure in terms of area and power consumption. In this experiment, you will build a current mirror source to supply a constant DC current using two ZVN3310 NMOS transistors in your parts kit. The circuit diagram for the current mirror source is shown in Figure 2. It contains two transistors Q1 and Q2 that are ideally identical as they have the same processing parameters (V_t , K_n , γ , ...) Typically, VLSI designers adjust the W/L ratio for each transistor to provide desired bias current. In the circuit shown, Q1 acts as a reference transistor that provides I_{Ref} through R which biases the gate voltage to some determined value V_G . The gate voltage is reflected to Q2 which acts as the biasing current source that biases the circuit. The current of Q2 (the bias current) is adjusted by designing the proper W/L ratio of Q2. The current in Q2 is determined by the following equations

$$\frac{I_2}{I_1} = \frac{\frac{1}{2} K'_n \left(\frac{W}{L}\right)_2 (V_{GS} - V_T)^2 (1 + \lambda V_{DS2})}{\frac{1}{2} K'_n \left(\frac{W}{L}\right)_1 (V_{GS} - V_T)^2 (1 + \lambda V_{DS1})} = \frac{\left(\frac{W}{L}\right)_2 (1 + \lambda V_{DS2})}{\left(\frac{W}{L}\right)_1 (1 + \lambda V_{DS1})} \approx \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1},$$

which can be expressed as

$$I_2 \approx \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} I_1. \quad (6)$$

Hence, you can easily design I_2 by controlling the size of the transistors. In this experiment, the two ZVN3310 NMOS transistors might *not* be perfectly matched, i.e., their K_n , V_t , and W/L might *not* be equal, so you will build the current mirror and then measure the ratio I_2 / I_1 .

Pre-lab:

- (a) Design the resistor R (between V_{DD} and drain of Q1) to provide drain current $I_{ref} = 1\text{mA}$ through NFET Q1. Assume that $V_{DD} = 5\text{V}$, $K_n = 0.08 \text{ A/V}^2$, $V_T = 1.7 \text{ V}$, and $\lambda = 0$ (i.e., we neglect the effect of λ since it is much less than 1).

 


Figure 2 Current mirror source.

Lab Procedures:

1. Using two ZVN3310 NMOS transistors (one for Q_1 and one for Q_2), construct the current mirror circuit of Figure 2 with a reference current $I_{Ref} = 1$ mA and $V_{DD} = 5$ V.
2. Very important: 1) Recheck all connections before applying power to the circuit. 2) When power is first applied, check the current draw on the power supply; if you see any current reading over 20 mA, immediately switch off the supply and recheck your circuit, in order to prevent burning out the either of the ZVN3310s.
3. For the resistor R , use a potentiometer (pot) or resistor box to provide variable resistance, and vary the resistance (starting from the value of R you designed in the pre-lab) until $I_{Ref} = 1$ mA.
4. Measure your currents I_{Ref} and I_{Bias} using the DMM and record them in your lab notebook, along with the ratio I_{Bias} / I_{Ref} .
5. Demonstrate your circuit to the TA and have them initial your lab checklist.

III. CMOS Inverter

CMOS technology uses NMOS and PMOS transistors that act as complementary switching transistors on the same wafer (substrate) or chip. The complementary transistors work in a push-pull mechanism such that when one transistor is ON then it becomes a short circuit, but when it is OFF it acts as open circuit. The push-pull switching mechanism is useful in building digital circuits. The simplest digital CMOS circuit is the inverter which is made of a PMOS transistor and an NMOS transistor as shown in Figure 3.

Lab Assignment 8: MOSFET Amplifier Circuits

When the CMOS inverter's input V_i is zero (logical low) then the NMOS transistor is OFF ($V_{GSn} < V_{tn}$) but the PMOS transistor is ON ($V_{SGp} > |V_{tp}|$) and $I_D = 0$ because NMOS is off. Since $I_D = 0$ and PMOS is ON, then the PMOS is operating in the triode region and $V_{SDp} = 0$ which implies $V_o = V_{Dp} = V_{Sp} = V_{DD}$ or Logical High. Similarly, when $V_i = V_{DD}$ (logical High) then the NMOS is ON, PMOS is OFF and $I_D = 0$ because PMOS is OFF. Hence, the NMOS is in the Triode region and $V_{DSn} = 0$ which implies that $V_D = V_S = V_o = 0$ (logical Low).

During the transition from 0 V (low) to V_{DD} (high), the CMOS inverter transitions through five operating regions as shown in Figure 3; these regions are summarized in Table 1. Note that the current is non-zero when the output of the inverter is transitioned; hence, the power dissipation is non-zero. This explains why the power dissipation is proportional to switching frequency. Note that in Region 3 $\left| \frac{dV_o}{dV_i} \right|$ is maximum, so it acts as an amplifier. In this experiment, you will build a CMOS inverter and you will investigate the different regions of the inverter. Then you will bias the inverter in Region 3 and test it as an amplifier.

Table 1 Summary of the five CMOS inverter transition regions

	NMOS	PMOS	V_i	I_D	V_o
Region 1	OFF	Triode	LOW	0	High V_{DD}
Region 2	Saturation	Triode	LOW	Small	High $\approx V_{DD}$
Region 3	Saturation	Saturation	Medium	High	Mixed $> 0 \text{ \& } < V_{DD}$
Region 4	Triode	Saturation	High	Small	Low $\approx V_{DD}$
Region 5	Triode	OFF	High	0	Low (0 V)

 


Figure 3 CMOS inverter

 


Figure 4 The voltage transfer curve of CMOS inverter

Lab Assignment 8: MOSFET Amplifier Circuits

Lab Procedures:

1. Set up the CMOS inverter circuit shown in Figure 3. Use the ZVN2110A NMOS transistor and the ZVP2110A PMOS transistor to build the circuit. Use one supply voltage to be V_{DD} and set $V_{DD}=5\text{ V}$, and the other DC supply voltage to be the DC input voltage.
2. *Very important: Recheck your circuit before applying power, and immediately shut off the power if the current draw is more than 10 mA.*
3. Using computer software such as MS Excel or Matlab, plot the voltage transfer curve (V_o vs. V_i) by varying the input voltage from 0 to 5 Volts. You may use the DMMs to measure your data points. You should get a curve that is similar to that shown in Figure 4.
4. Determine the five transition regions of CMOS inverter, similar to those in Figure 4.
5. *Demonstrate your circuit and your transition curve to the TA and have him or her initial your lab checklist.*
6. In region 3, both transistors are saturated, $\frac{dV_o}{dV_i}$ is maximum, and the inverter acts as an amplifier. At the input, use the function generator to apply a 10 mV peak-to-peak sine wave at 1 kHz. Slowly adjust the offset voltage of the function generator until V_o is centered at $\frac{1}{2} V_{DD}= 2.5\text{V}$. At this point, the peak-to-peak output voltage swing is maximum. Determine the gain of the amplifier at this point.
7. *Demonstrate your circuit and gain to the TA and have him or her initial your lab checklist.*

Lab Report:

In your lab report, provide a summary of the results of this lab assignment. You should include, at a minimum, all items indicated on the lab checklist. Append the lab checklist sheet with Laboratory Instructor's initials indicating completed lab demos to your report.

Appendix A: Components Packages and Pins Assignments

 


Figure A1. TO-92 Package for ZVN2210A, ZVN3310 and ZVP2110A and their pin assignments

Lab 8 Checklist

Name: _____

Lab title and introduction

(5 pts)

- Lab title, your name, date, and lab partner.
- Brief introduction (two or three sentences) explaining the purpose of this lab.

I. Single Stage MOSFET Amplifier (45 pts total)

1. Diagram of amplifier. (2 pts)

2. Measured component values: R_1 , R_2 , R_S , R_D , R_L , C_G , C_D , C_S (3 pts)

3. Measured DC voltages: V_G , V_S , V_D , I_D (5 pts)

4. Measured mid-band gain. (5 pts)

_____ 5. **DEMO:** Have a TA initial this sheet, indicating that he/she has observed your circuit's mid-band gain operation. (5 pts)

6. Measured values of upper and lower corner frequencies. (5 pts)

7. Table of measured values of gain vs. frequency. (5 pts)

8. Plot of measured gain vs. frequency. (5 pts)

9. Maximum peak-to-peak output swing. (5 pts)

_____ 10. **DEMO:** Have a TA initial this sheet, indicating that he/she has observed your circuit's frequency response operation. (5 pts)

II. Current Mirror Source (20 pts total)

1. Diagram of current mirror circuit. (5 pts)

2. Table of measured values of I_{Ref} and I_{Bias} and the ratio I_{Bias} / I_{Ref} ; compare I_{Ref} with its expected value. (5 pts)

_____ 3. **DEMO:** Have a TA initial this sheet, indicating that he/she has observed your circuit's operation. (10 pts)

III. CMOS Inverter (30 pts total)

1. Diagram of CMOS inverter. (5 pts)

2. Table of measured V_i vs. V_o for the voltage transfer curve. (5 pts)

3. Plot the voltage transfer curve. (5 pts)

_____ 4. **DEMO:** Have a TA initial this sheet, indicating that he/she has observed your circuit's operation and your voltage transfer curve. (5 pts)

5. Measured amplifier gain at the midpoint of V_o . (5 pts)

_____ 6. **DEMO:** Have a teaching assistant initial this sheet, indicating that they have observed your circuit's operation as an amplifier. (5 pts)